

AC Sweep simulation

Jiarui Huang(黄家睿)

202283890036

Introduction and Aim


This experiment explores the behaviour of a simple RC (Resistor-Capacitor) circuit and understand its response to changes in input voltage. To achieve this, we will use a linear potentiometer as a variable resistor in the circuit. A potentiometer, often referred to as a pot, is a three-terminal resistor with an adjustable tap that allows us to change the resistance value along its length. In this experiment, we will utilize a linear potentiometer to vary the resistance in the RC circuit. By adjusting the potentiometer, we can control the rate at which the capacitor charges and discharges, thus influencing the time constant and the behaviour of the circuit.

Theory


the cut-off frequency f_c is defined the point at which the output voltage is equal to -3 dB (or 70%) of the input voltage, where:

$$f_c = \frac{1}{2\pi RC}$$

Circuit Diagram

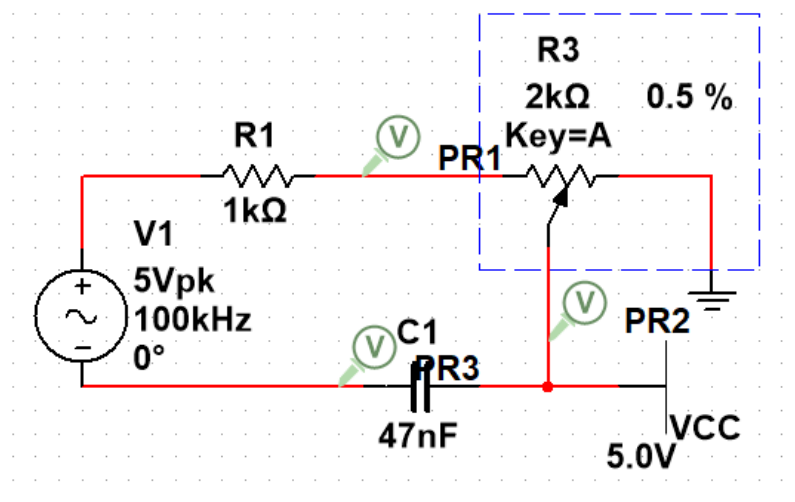

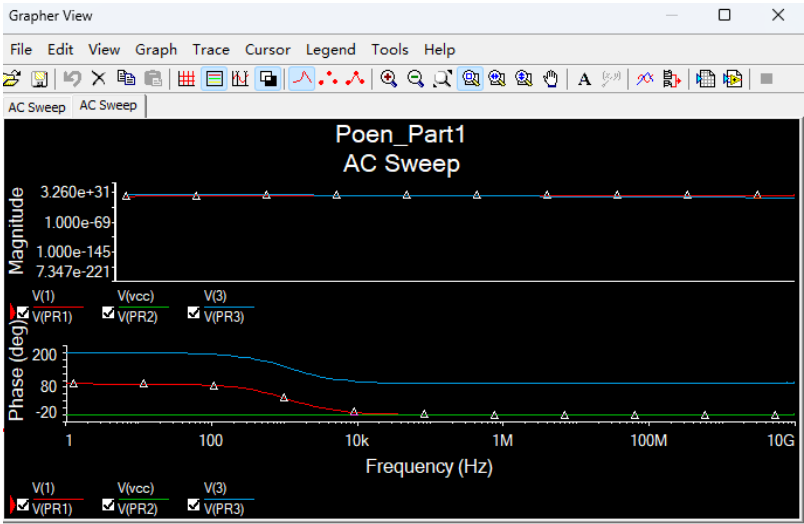The output of the AC sweep simulation This diagram show the the circuit's response and determine the cut-off frequency with the potentiometer of 0.5%.



This diagram show the the circuit's response and determine the cut-off frequency with the potentometer of 100%.

